

No announcements today

---

Recall:


Kirchoff's laws for electrical circuits

Source: Postnikov lecture notes

(link on 412 course website)

Let  $G$  be a (loopless) graph, and consider edges of  $G$  to represent resistors.

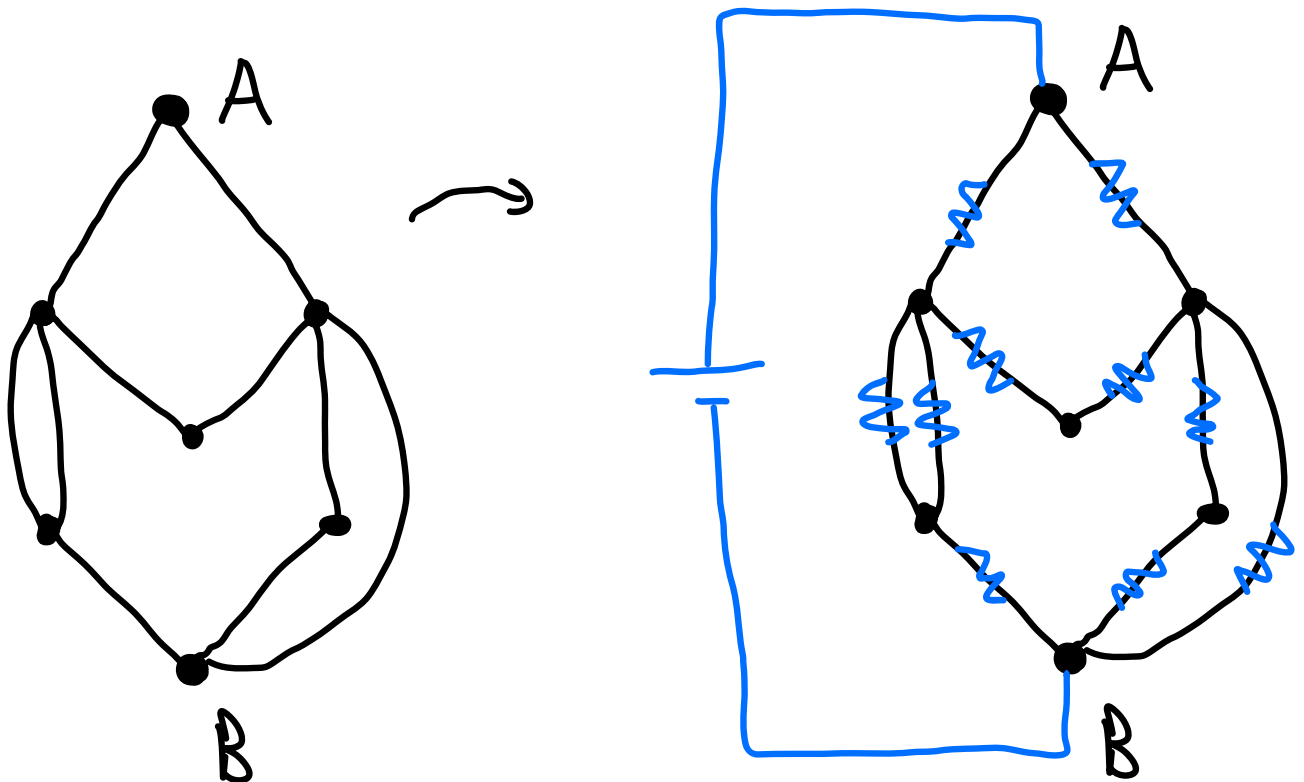Choose vertices  $A$  and  $B$  to be connected to a source of electricity



Choose any orientation  $D$  of  $G$   
(doesn't matter which)

Quantities associated to each edge  $e$ :

- Current  $I_e$  through  $e$
- Voltage (or potential difference)  $V_e$  across  $e$
- Resistance  $R_e$  of  $e$  ( $R_e > 0$ )
- Conductance  $C_e := \frac{1}{R_e}$

Three laws:

K1: At any vertex  $v$ , the sum of the in-currents equals the sum of the out-currents:

$$\sum_{\substack{e \text{ has} \\ \text{head } v}} I_e = \sum_{\substack{e \text{ has} \\ \text{tail } v}} I_e$$

K2: For any cycle  $C$  in  $G$ , the (signed) sum of voltages is 0:

$$\sum_{e \in E(C)} \pm V_e = 0,$$

where we traverse  $C$  in either direction, and the term involving  $V_e$  is positive iff we traverse  $e$  in the way it's oriented in  $D$ .

Ohm's Law:  $\forall e \in E(D)$ ,

$$V_e = I_e R_e \quad (I_e = V_e C_e)$$

Prop:  $K_2$  is equivalent to the following condition:

$K_2'$ : There exists a (unique) function

$$U: V(G) \rightarrow \mathbb{R},$$

called the potential function, s.t.


$$a) \quad \forall \quad \overset{u}{\bullet} \xrightarrow{e} \overset{v}{\bullet}, \quad V_e = U(v) - U(u)$$

$$b) \quad U(B) = 0$$

Pf: Homework!

Goal: find the "effective resistance"  $R(G)$   
of a whole graph  $G$

Ex:

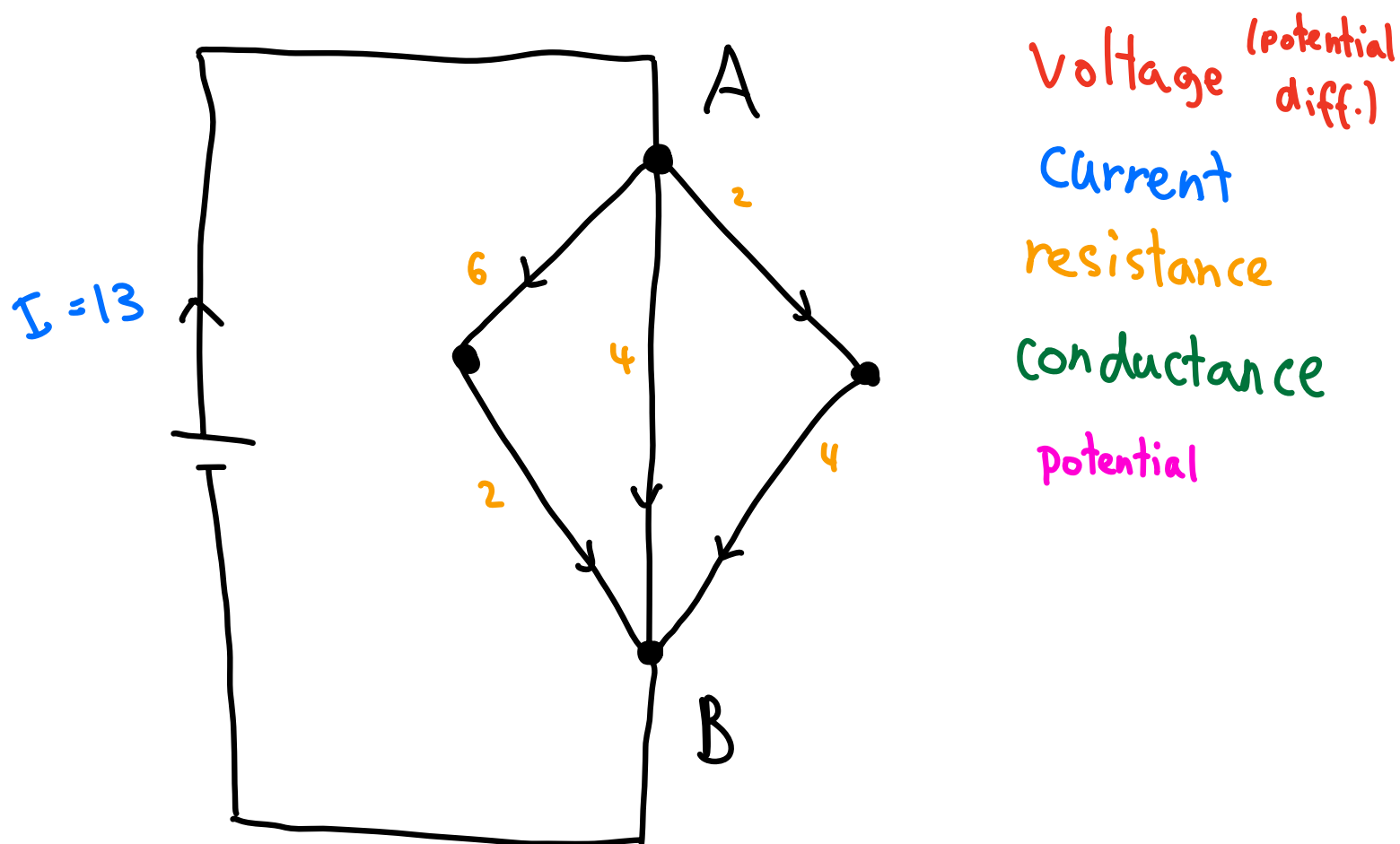

The graph  $G$  has

total potential difference  $V =$

resistance  $R =$

conductance  $C =$

Lets combine our three laws: ( $v$  fixed)

$$K_1: \sum_{\substack{e \text{ has} \\ \text{head } v}} I_e = \sum_{\substack{e \text{ has} \\ \text{tail } v}} I_e$$

Apply Ohm's Law:

$$\sum_{\substack{e \text{ has} \\ \text{head } v}} \frac{V_e}{R_e} = \sum_{\substack{e \text{ has} \\ \text{tail } v}} \frac{V_e}{R_e}$$

$$\sum_{\substack{e \text{ has} \\ \text{head } v}} V_e C_e = \sum_{\substack{e \text{ has} \\ \text{tail } v}} V_e C_e$$

$$\text{Apply } K_2': V_e = U(\text{head}) - U(\text{tail})$$

$$\sum_{\substack{u \xrightarrow[e]{\quad} v \\ \text{in } D}} (U(v) - U(u)) C_e = \sum_{\substack{v \xrightarrow[e]{\quad} u \\ \text{in } D}} (U(u) - U(v)) C_e$$

Rearrange:

$$\sum_{\substack{u \xrightarrow{e} v \\ \text{in } G}} (V(v) - V(u)) c_e = 0$$

Actually, need to treat A, B differently:

$$\sum_{\substack{u \xrightarrow{e} v \\ \text{in } G}} (V(v) - V(u)) c_e = \begin{cases} -1, & \text{if } v = A \\ 1, & \text{if } v = B \\ 0, & \text{otherwise} \end{cases}$$

Rearrange some more

$$V(v) \left( \sum_{\substack{u \xrightarrow{e} v \\ \text{in } G}} c_e \right) - \sum_u V(u) \left( \sum_{\substack{u \xrightarrow{e} v \\ \text{in } G}} c_e \right) = \begin{cases} -1, & A \\ 1, & B \\ 0, & \text{else} \end{cases}$$

Surprise — this is matrix multiplication

Order  $V(G)$  as  $v_1 = A, v_2, \dots, v_n = B$

$$\text{Let } \vec{u} = \begin{bmatrix} U(v_1) \\ \vdots \\ U(v_n) \end{bmatrix} \quad \vec{i} = \begin{bmatrix} -I \\ 0 \\ \vdots \\ 0 \\ I \end{bmatrix}$$

Then  $K\vec{u} = \vec{i}$ , where

$$K_{ij} = \begin{cases} \sum_{\substack{e \text{ } \overline{v_i} \\ \text{in } G}} c_e, & \text{if } i=j \\ \sum_{\substack{v_j \text{ } \overline{e} \text{ } v_i \\ \text{in } G}} c_e, & \text{if } i \neq j \end{cases}$$

$K = L(G)$ , the (weighted) Lagrangian matrix of  $G$ !



The weight  $wt(e) = C_e$ , the conductance of  $e$

How do we find the effective resistance  $R$ ?

Use Ohm's Law:

$$R = \frac{V}{I} = \frac{U_1 - U_n}{I}$$

Shifting & scaling, take  $U_1 = 0$ ,  $I = 1$ , so

$$R = U_n = \begin{matrix} \text{last} \\ \text{entry} \\ \text{of} \end{matrix} L(G)^{-1} \begin{bmatrix} -1 \\ 0 \\ \vdots \\ 0 \\ 1 \end{bmatrix}$$

$$= \begin{matrix} \text{last} \\ \text{entry} \\ \text{of} \end{matrix} L^1(G)^{-1} \begin{bmatrix} 0 \\ \vdots \\ 0 \\ 1 \end{bmatrix}$$

By Cramer's Rule (applied to this situation):

$$V_n = \frac{\det L^{1,n}(G)}{\det L^1(G)}$$

By the Matrix Tree Theorem:

$$\det L^1(G) = \tau(G)$$

$$\det L^{1,n}(G) = \det L^1(\tilde{G}) = \tau(\tilde{G})$$

$$\text{where } \tilde{G} = (G \sqcup AB) \cdot AB$$


(glue A and B together)

We have proven the following:


Theorem (Kirchoff):

$$R(G) = \frac{\tau(\tilde{G})}{\tau(G)}$$


Ex:

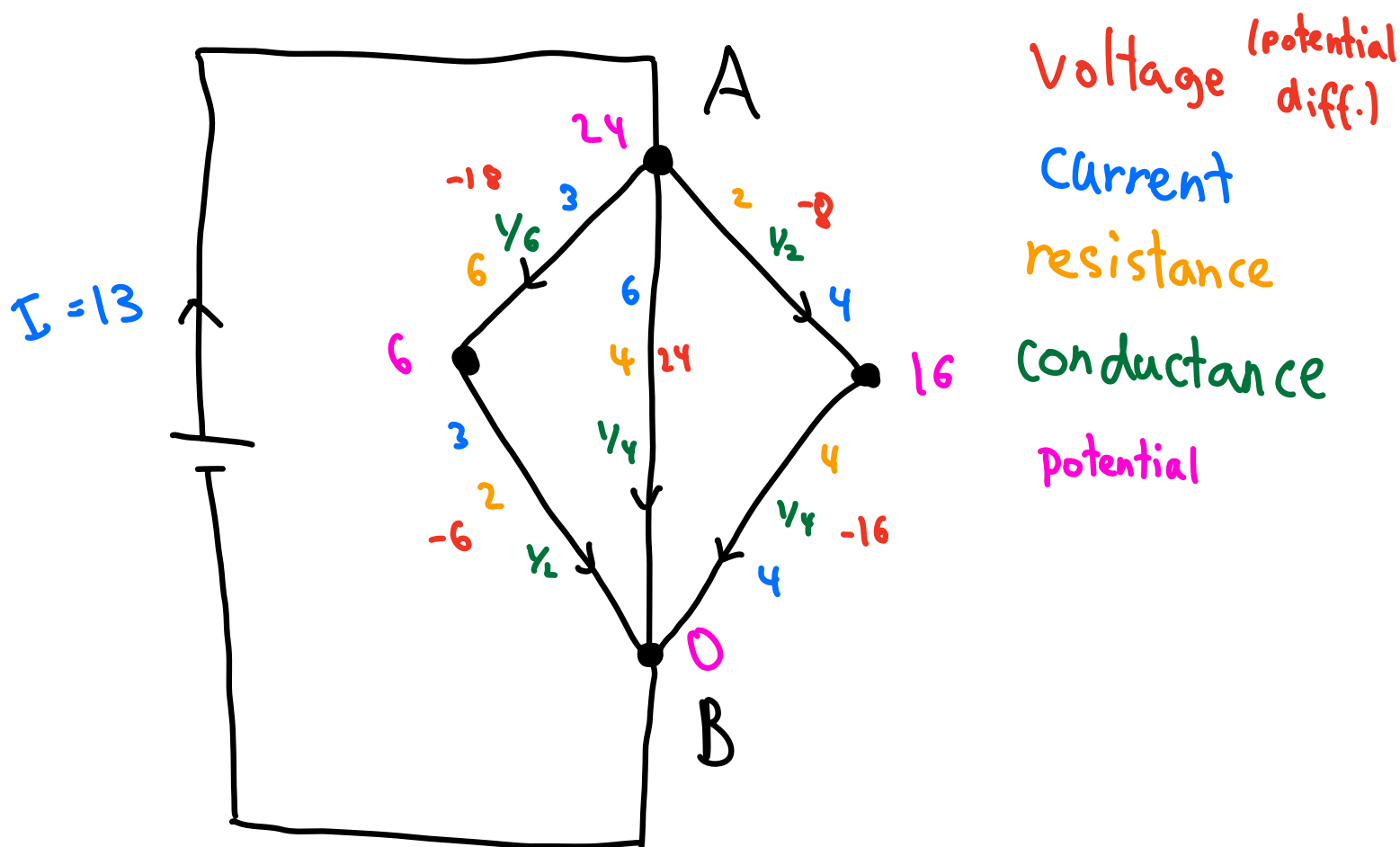


G:

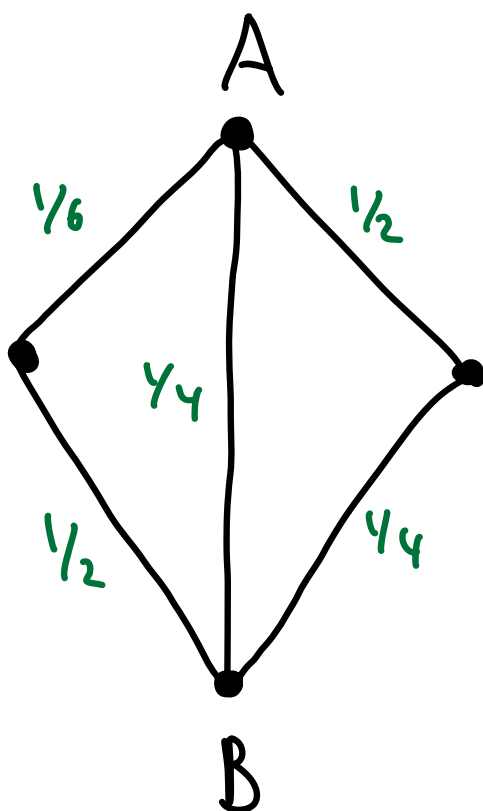


$\tilde{G}$ :

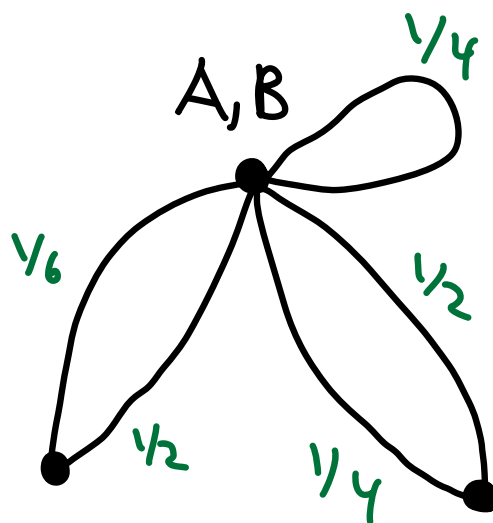


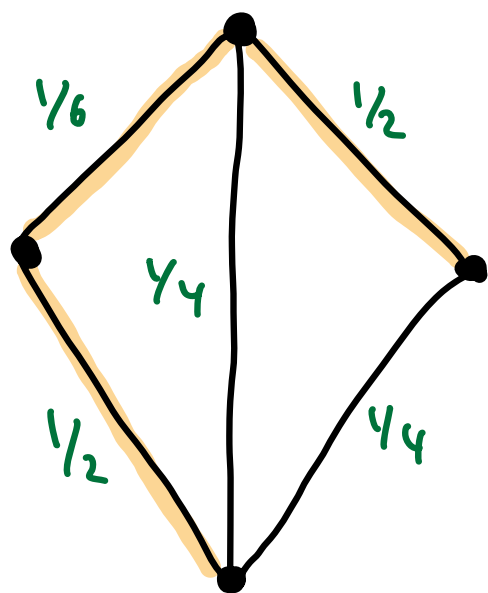


$$\frac{1}{24}$$

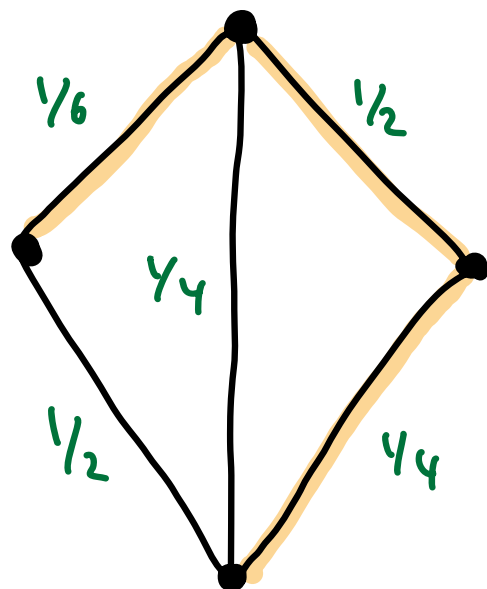


$$\frac{1}{48}$$

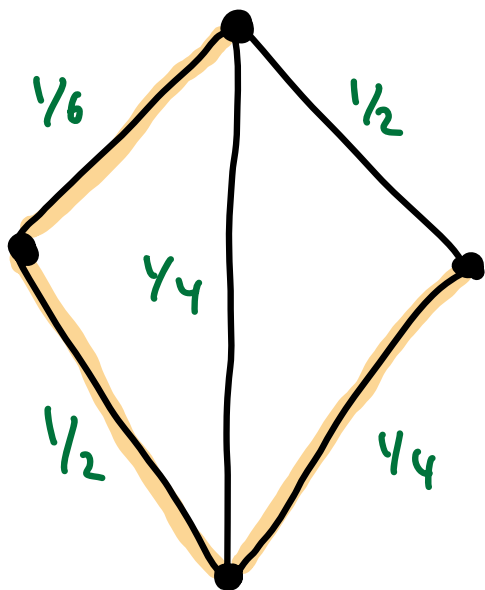


$$\frac{1}{48}$$

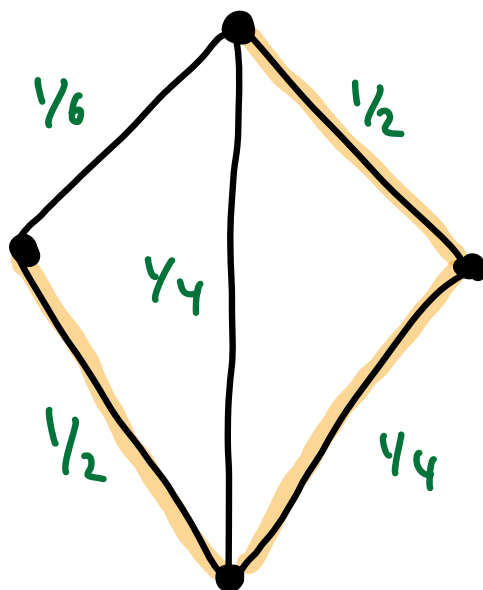


$$\frac{1}{16}$$

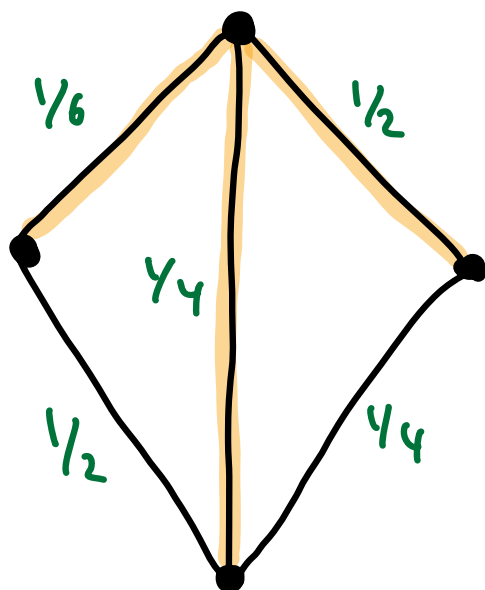


$$\frac{1}{48}$$

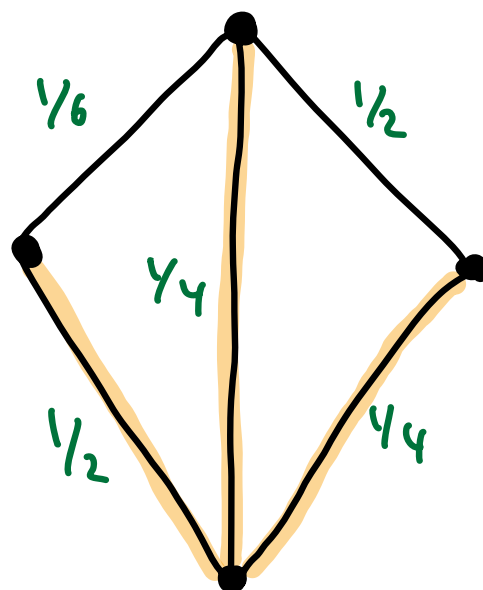

$$\frac{1}{32}$$

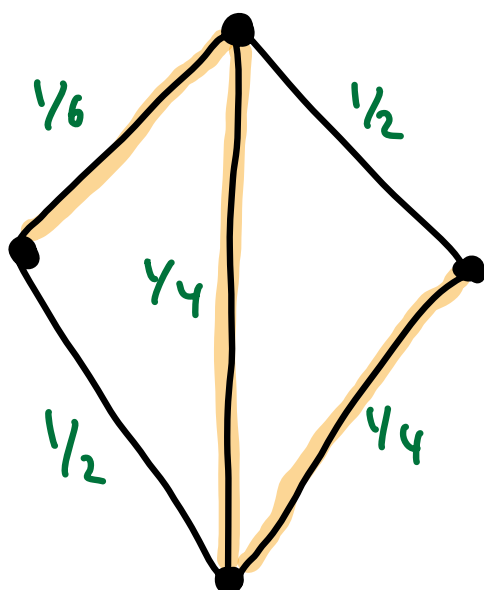


$$\frac{1}{96}$$

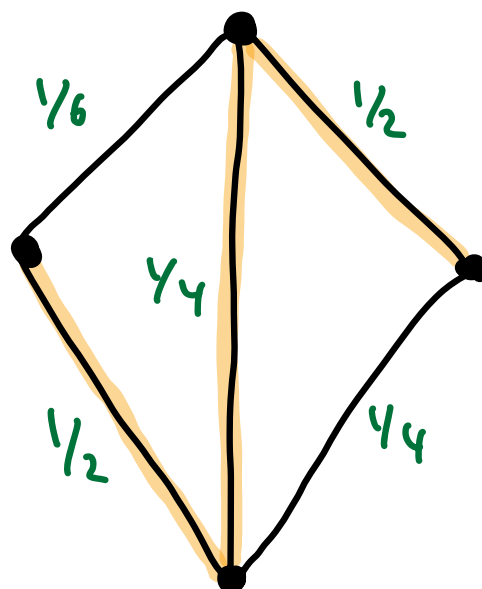


$$\frac{1}{16}$$


$$\tau(G) = \frac{13}{48}$$

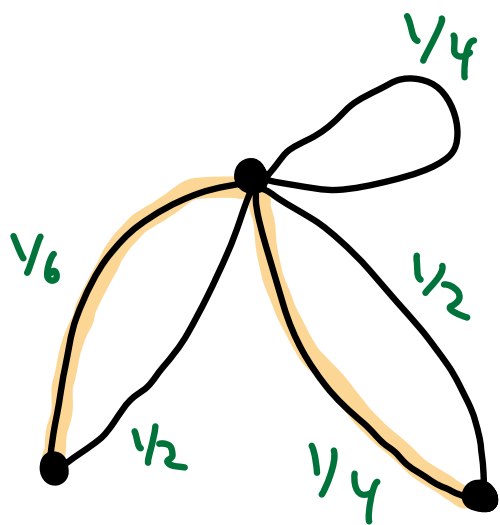


$$\frac{1}{24}$$

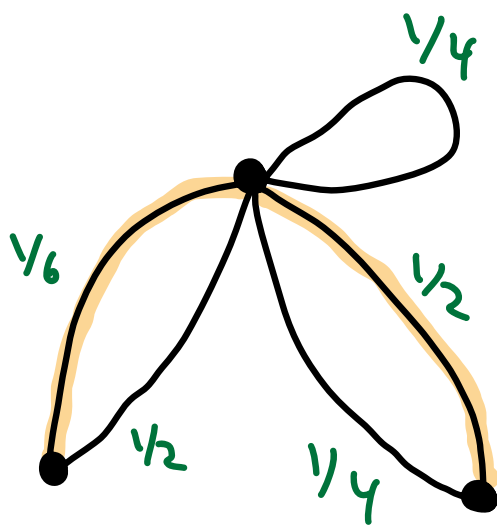

$$\frac{1}{12}$$

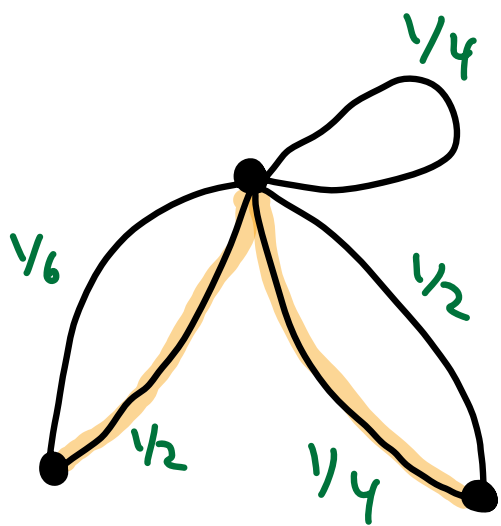

$$\frac{1}{8}$$

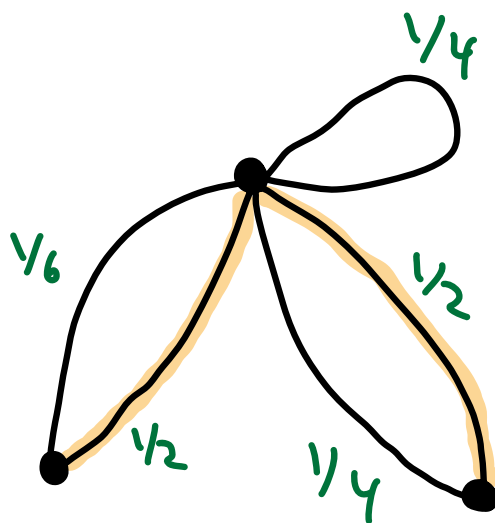

$$\frac{1}{4}$$

$$\tau(\tilde{G}) = \frac{1}{2}$$

$$R(G) = \frac{\tau(\tilde{G})}{\tau(G)} = \frac{24}{13} \quad \checkmark$$